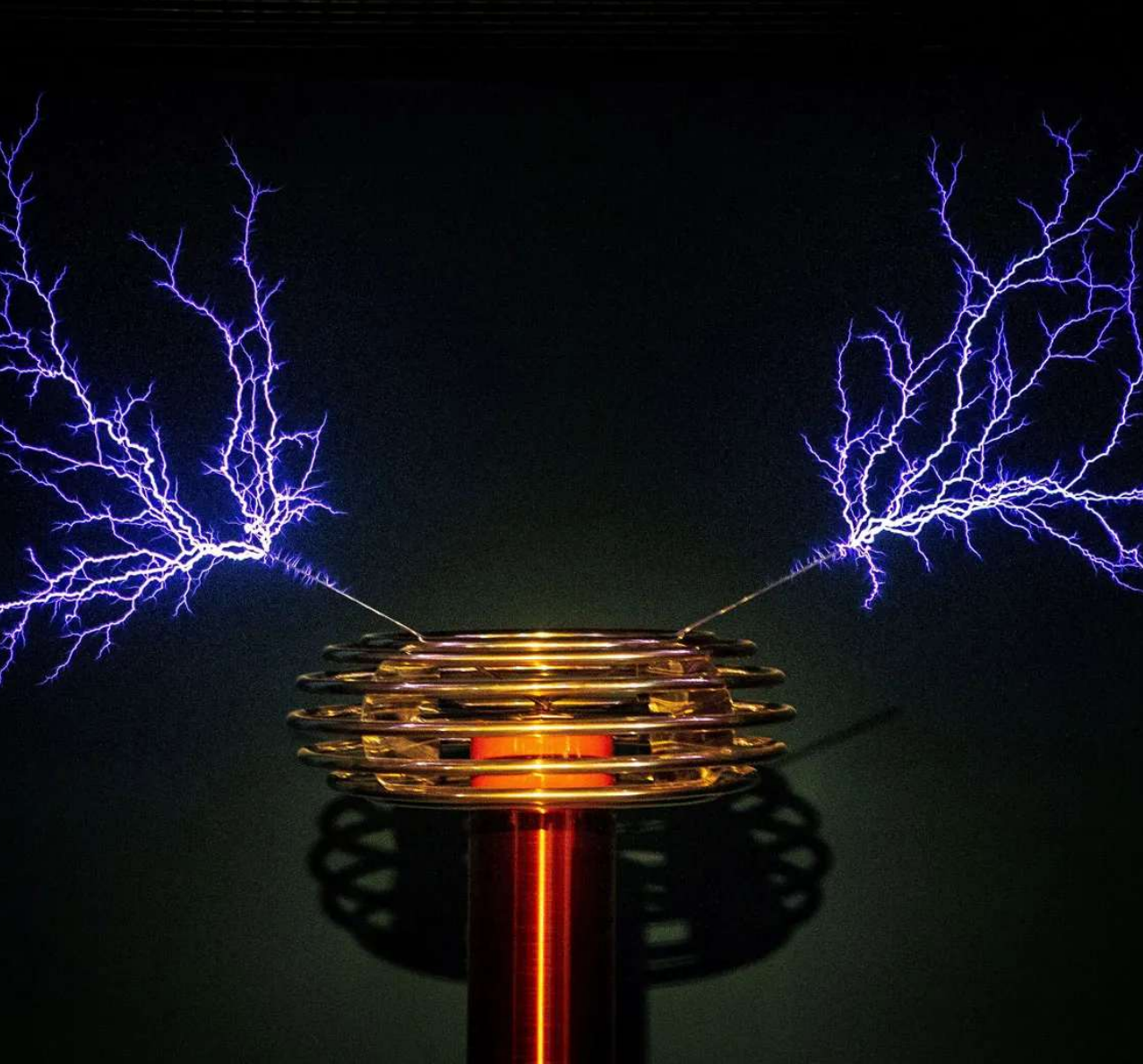




Solid-State Musical Tesla
Coils: Architecture,
Educational Uses, and High
Voltage

Alex Kowalewski
&
Zander Sellese

Research conducted at NC State
University under Dr. David Ricketts

About Me

- Callsign: KR4ESQ – General
- BS EE, NCSU, May 2025
- MS EE, NCSU, May 2026
- RF circuits + Analog Electronics



Past Work




Past Work



What is a Tesla Coil?

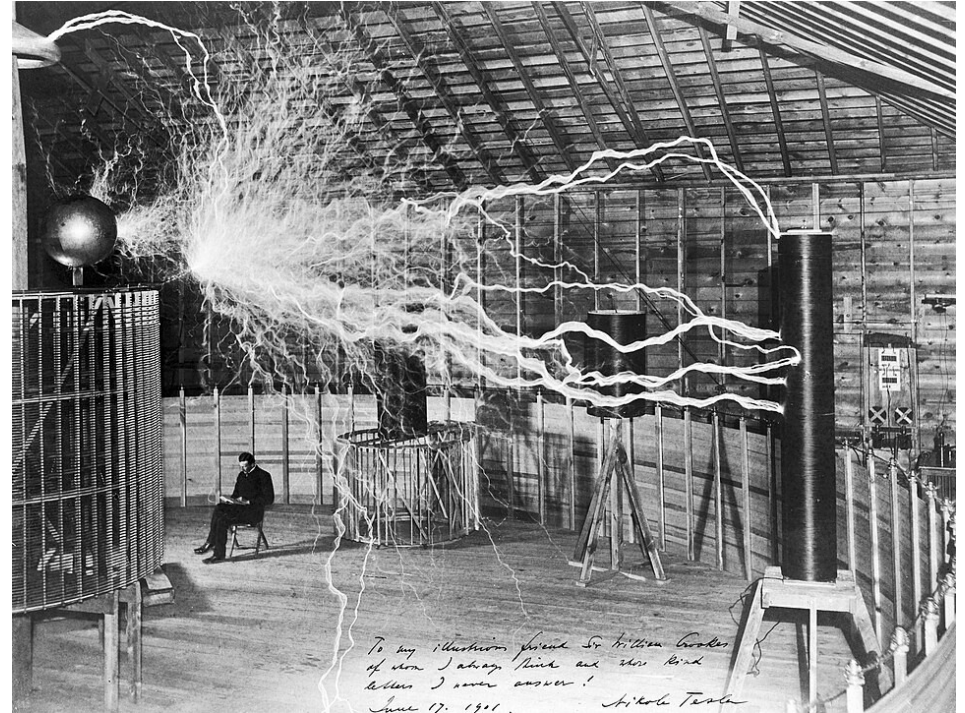- A cool demo of EM concepts?
- 
- Air-core resonant transformer driven by an oscillator
 - Typical resonant frequencies (F_{res}): 10s of kHz to 1MHz
 - Typical output voltages: 50kV to several million volts!



Nikola Tesla in his Colorado Springs lab circa 1899.
Fun Fact: this famous image is a double-exposure!

Types of Tesla Coils

Spark Gap (SGTC)



Griffith Observatory, Los Angeles

Spark
Length

???


Music
al
Contro
l

Early Solid State Tesla Coils (SSTC)



Loneoceans Laboratories


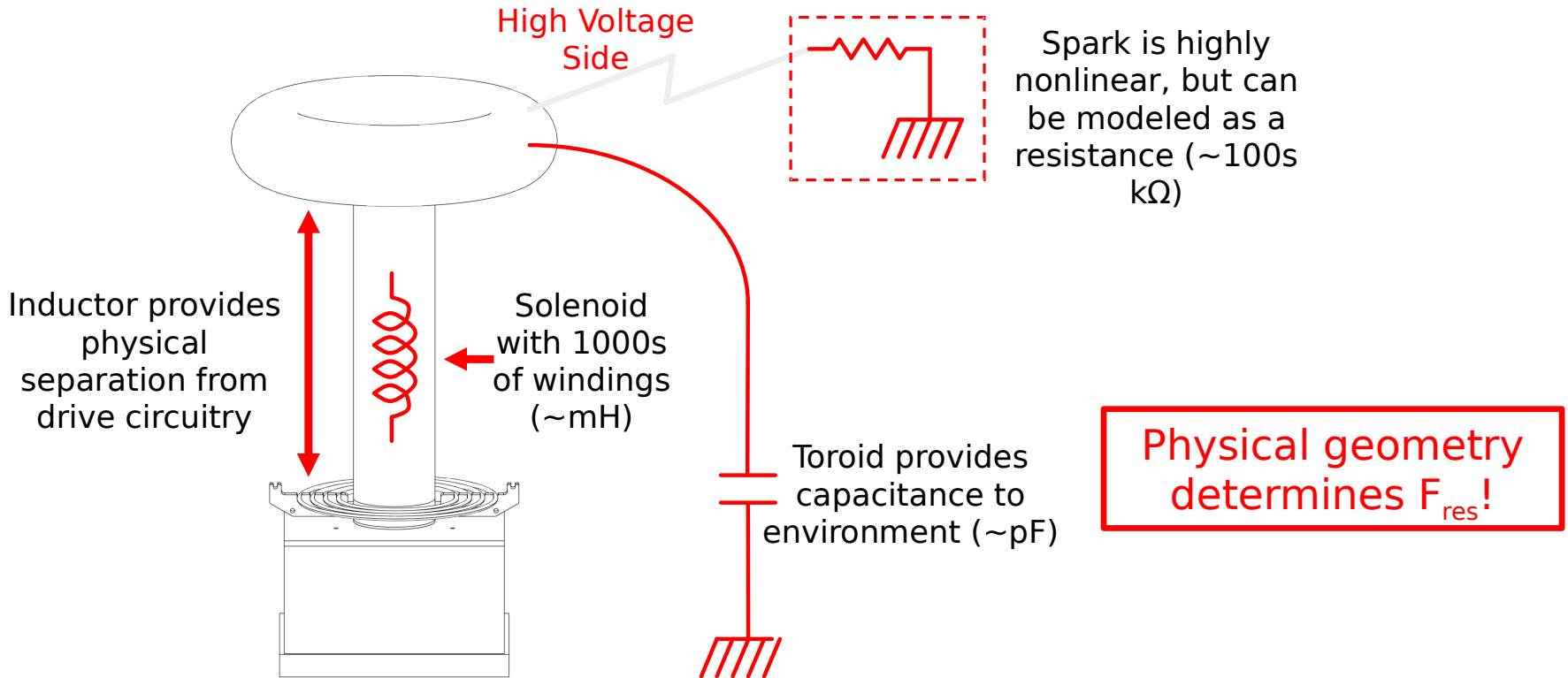
The Tesla Resonator – The “Heart” of the Tesla Coil



Resonant Network Design

- Driver: circuit able to excite network at F_{res}
 - R1 set by desired drive voltage/current (typically 100s of V and A $\rightarrow$ R1 $\sim \Omega$'s)
- Goal: Transfer maximum power to spark
- Helpful to think of design as an impedance matching problem.
 - Driver (Ω 's) $\rightarrow$ Spark (100s k Ω 's)

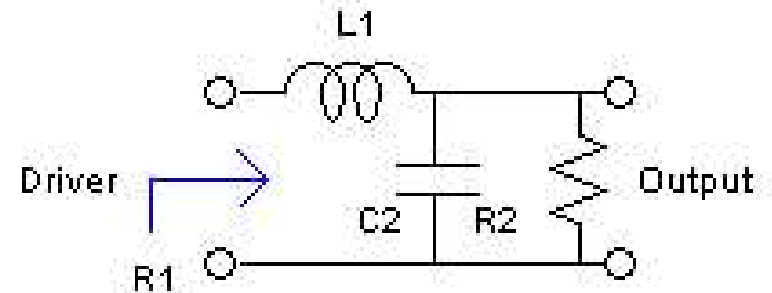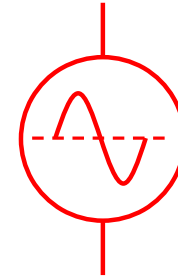Designing a Solid-State Tesla Coil, Antonio Carlos M. de Queiroz





Simple L-Match

Pros:

- Simple, closed form solution
- No additional matching components

Cons:

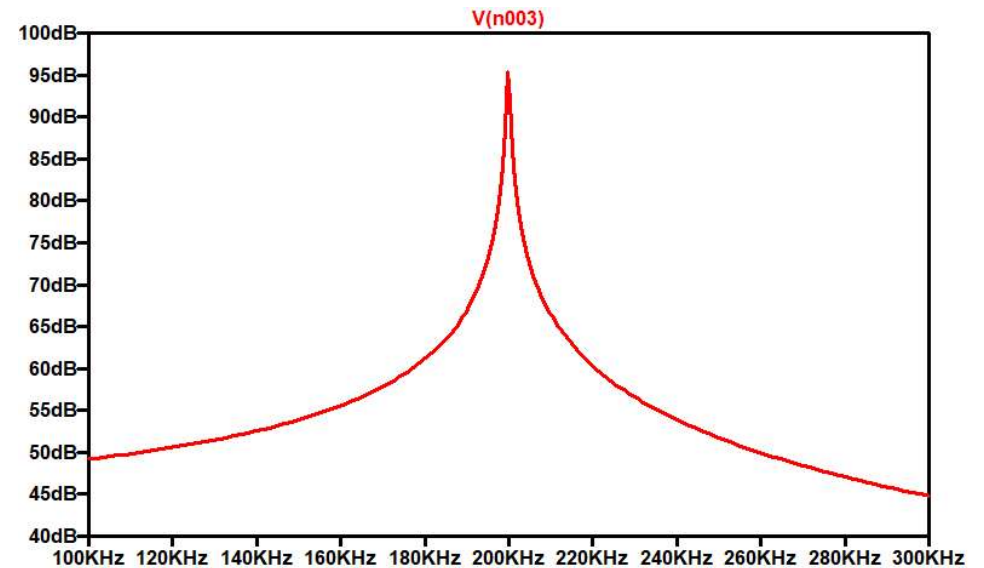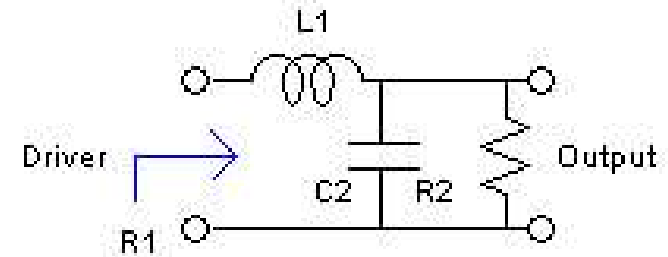- Sensitive to changes in R2 (R1 no longer purely resistive)
- Very high Q





Output voltage of example L network
(dBV),
 $F_{\text{res}} = 200 \text{ kHz}$

Designing a Solid-State Tesla Coil, Antonio Carlos M. de Queiroz

Impact of Q

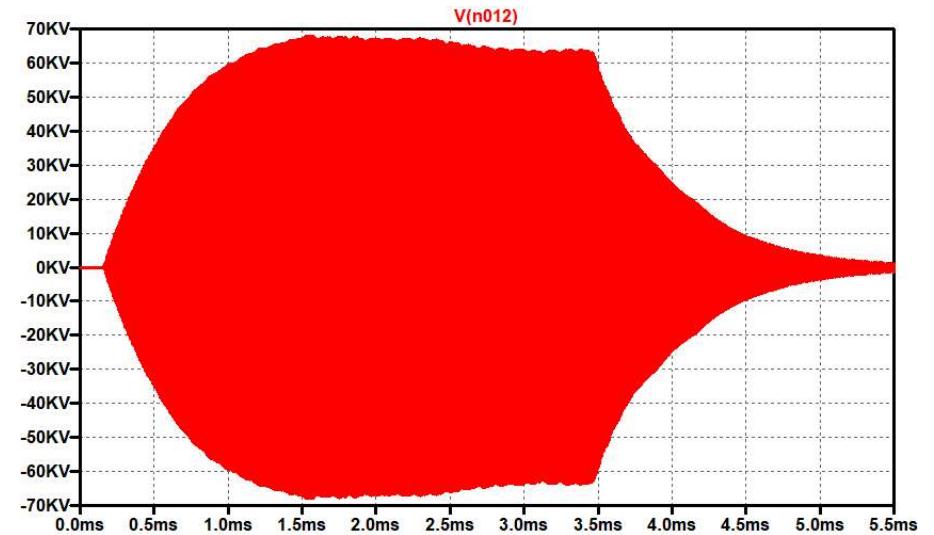
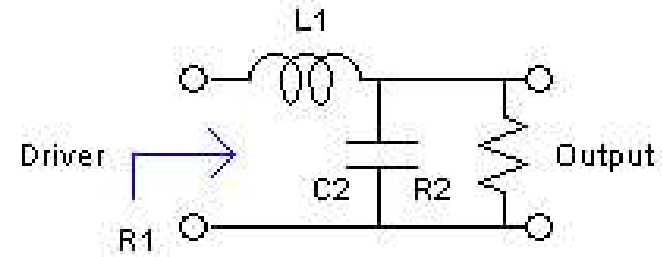
- High Q causes long ring-up time
 - Takes approx. Q cycles to reach steady state (~ms)
 - Challenging to build necessary driver
- Q set by R1 and R2
- If R1 is varied → Q proportional to voltage gain
 - How can we lower Q but maintain voltage gain?



Resonant ring-up of example L network, $F_{\text{res}} = 200$ kHz,
 $Q = 588$

Designing a Solid-State Tesla Coil, Antonio Carlos M. de Queiroz

Controlled Q Impedance Matching

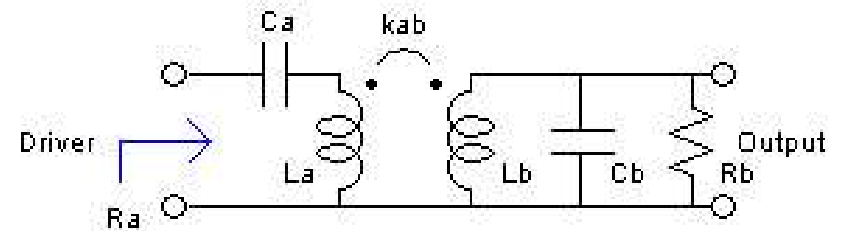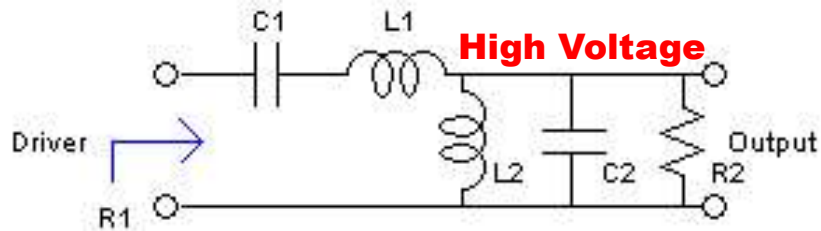

Bandpass Butterworth filter


- Offers precise control over bandwidth (and therefore rise time)
- Challenging to fabricate (due to HV)

Designing a Solid-State Tesla Coil, Antonio Carlos M. de Queiroz


Tuned Transformer

- Mathematically equivalent response
- k_{ab} typically 0.1-0.2 (loose coupling)
- Two LC Tanks → "Dual Resonant Solid State Tesla Coil" (DRSSTC)



Performance Comparison

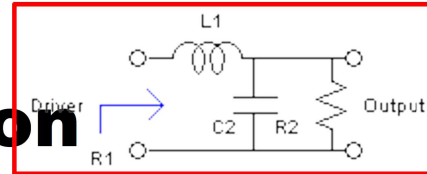

Q = 588

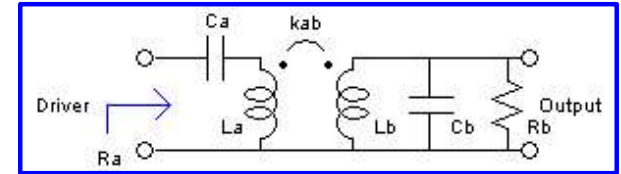

Q = 10



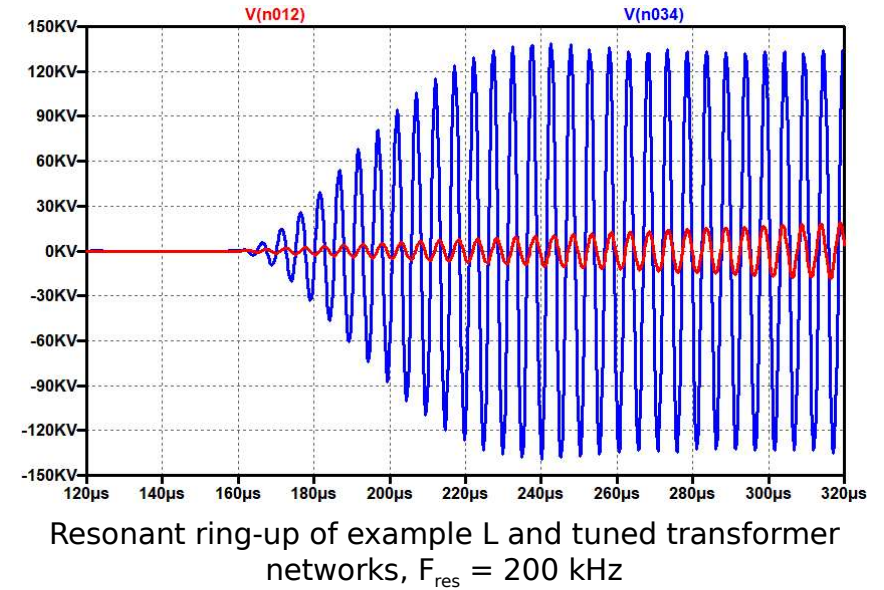
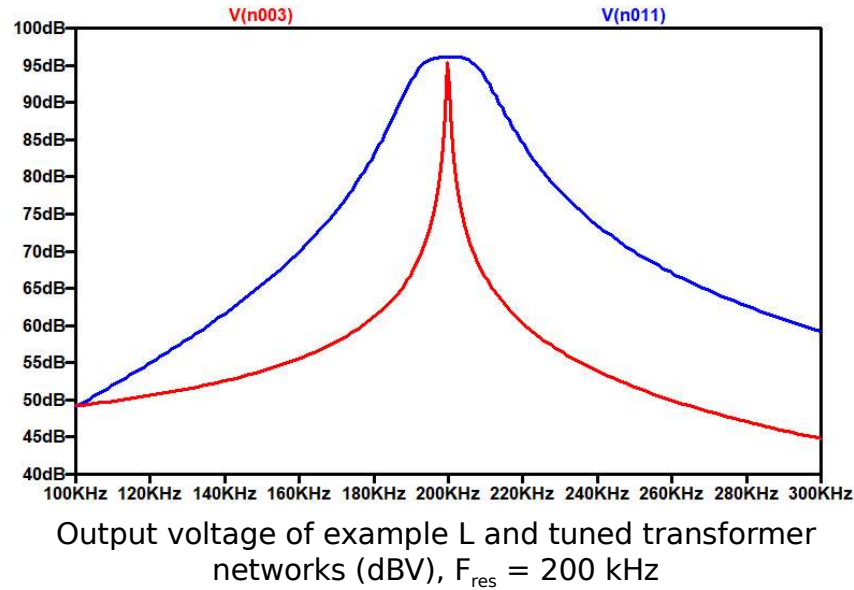


Tuned transformer achieves faster response without compromising gain!

Designing a Solid-State Tesla Coil, Antonio Carlos M. de Queiroz


Physical Construction

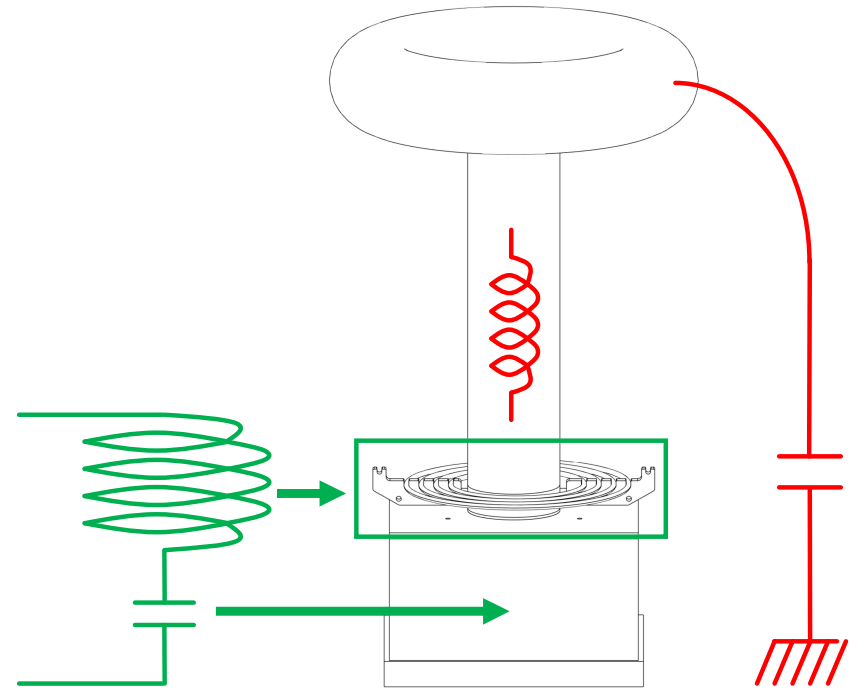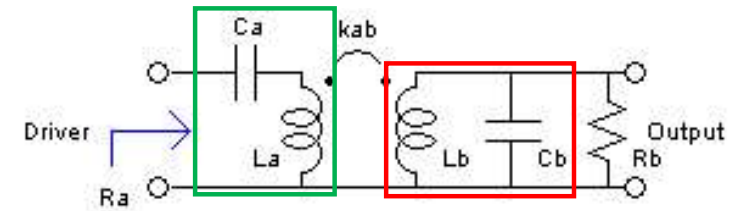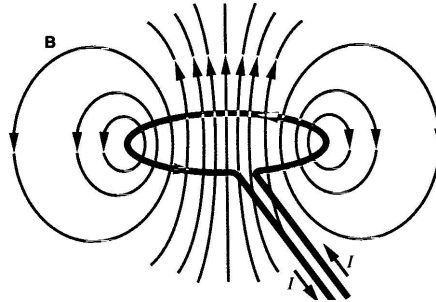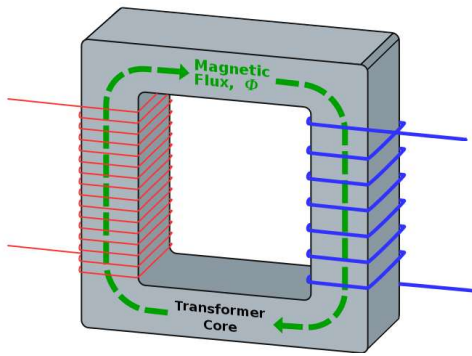- Stacked inductors
- k_{ab} controlled by coil size/spacing
 - Remember: typically only 0.1-0.2 (loose coupling)



Driving the Resonant Network

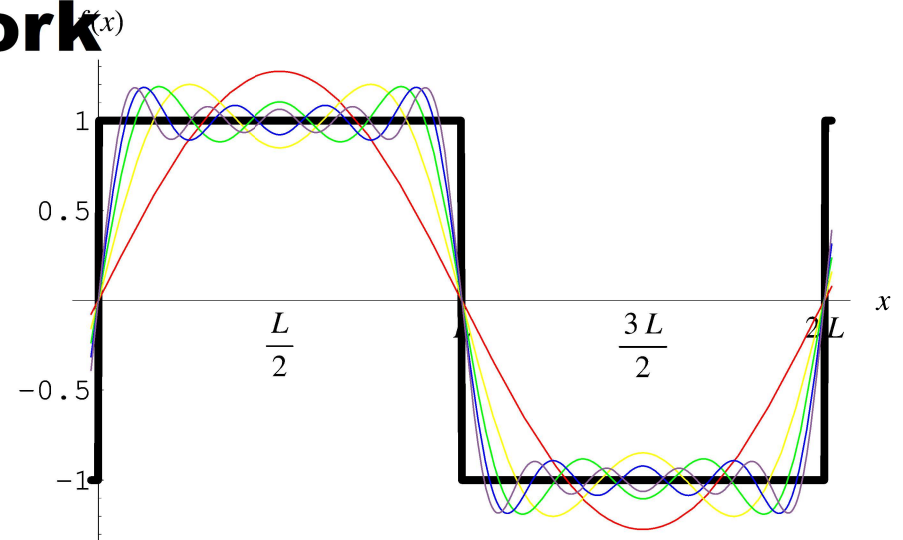
- Driver: circuit able to excite network at F_{res} (implied sinusoid)
- What if we use a square wave?
 - Narrowband network only passes fundamental frequency
 - Coefficient of $\frac{4}{\pi} \rightarrow$ “free” gain!



$$f(x) = \frac{4}{\pi} \sum_{n=1,3,5,\dots}^{\infty} \frac{1}{n} \sin\left(\frac{n\pi x}{L}\right).$$


Fourier Series--Square Wave, Weisstein, Eric W., From Wolfram Mathworld

Bridge Topologies

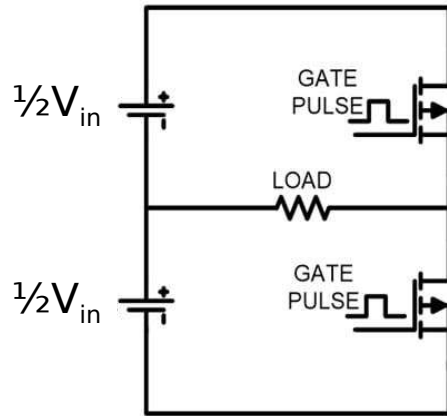

Half Bridge

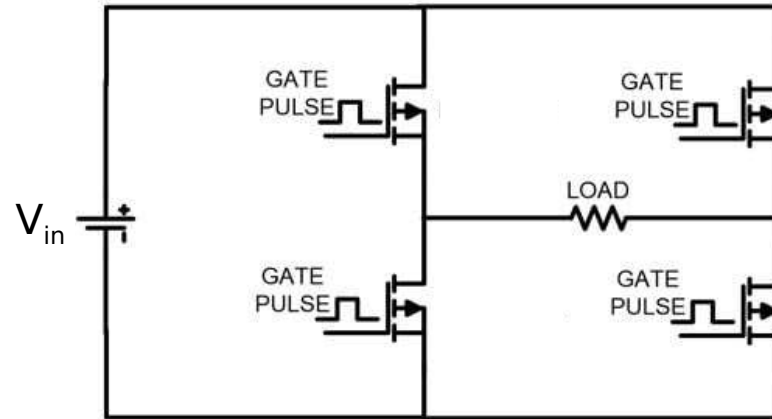- $V_{out} = \pm \frac{1}{2}V_{in}$
- 2 switching elements (lower cost)



Full Bridge (H-Bridge)


- $V_{out} = \pm V_{in}$ (higher power)
- 4 switching elements

Single Phase Half Bridge and Full Bridge Inverter using MATLAB, Ravi Kansagara


Minimizing Losses

- **Hard Switching:** device switched abruptly during high voltage/current condition
- **Soft Switching:** device switched at near-zero voltage/current to minimize losses
 - Zero Voltage/Current Switching (ZVS/ZCS)
 - Crucial...remember we are conducting 100s of Amps!

Hard Switching

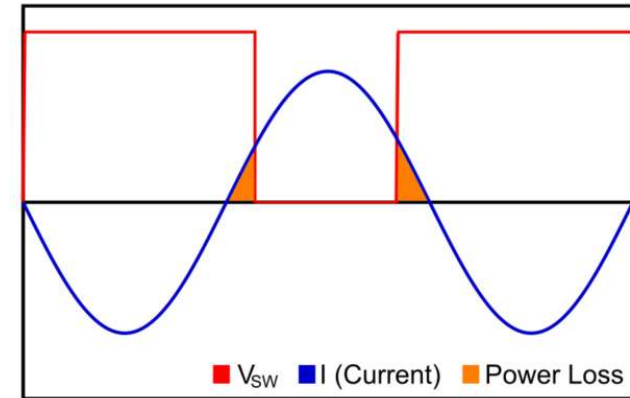


Soft Switching

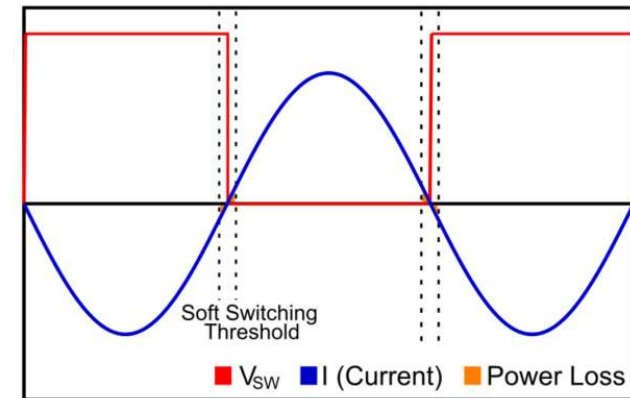

Practical ZVS/ZCS Implementation


- How can we switch at exact zero-crossings?
- **Solution 1:** Oscillator at our calculated F_{res}
 - F_{res} depends on environment, spark length, etc. → challenging to predict!
- **Solution 2:** Use feedback!
 - Current transformer/antenna
 - Can be taken from either LC tank
 - Driver adapts to F_{res}

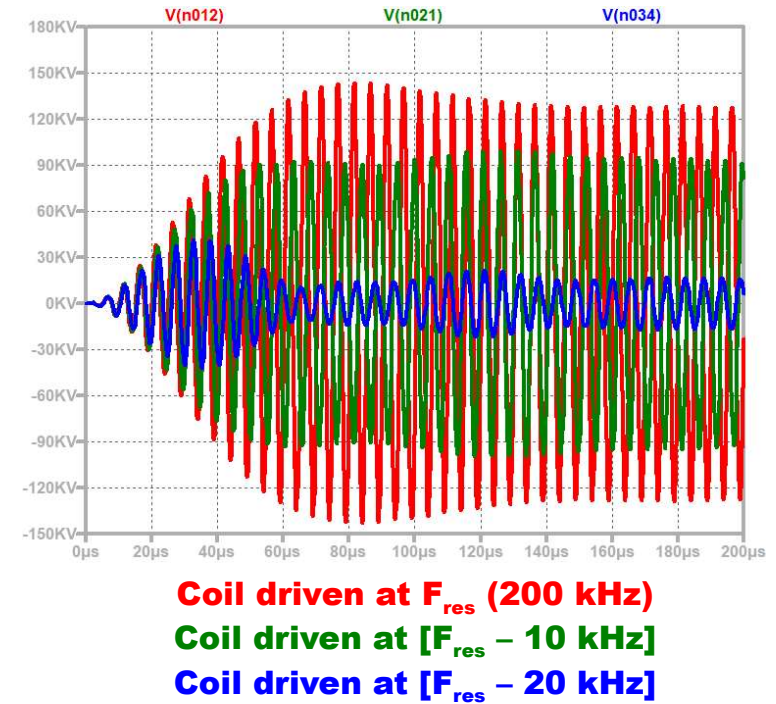Impact of Driving Frequency on Output Voltage



Feedback Driver

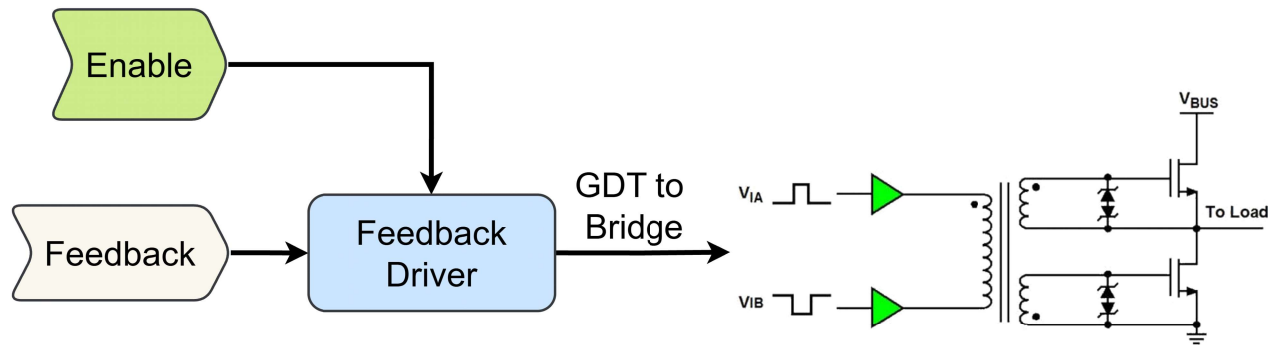
- Uses feedback to switch bridge at zero-crossings
 - 3 stages of operation



Feedback Driver

Stage 1: Startup

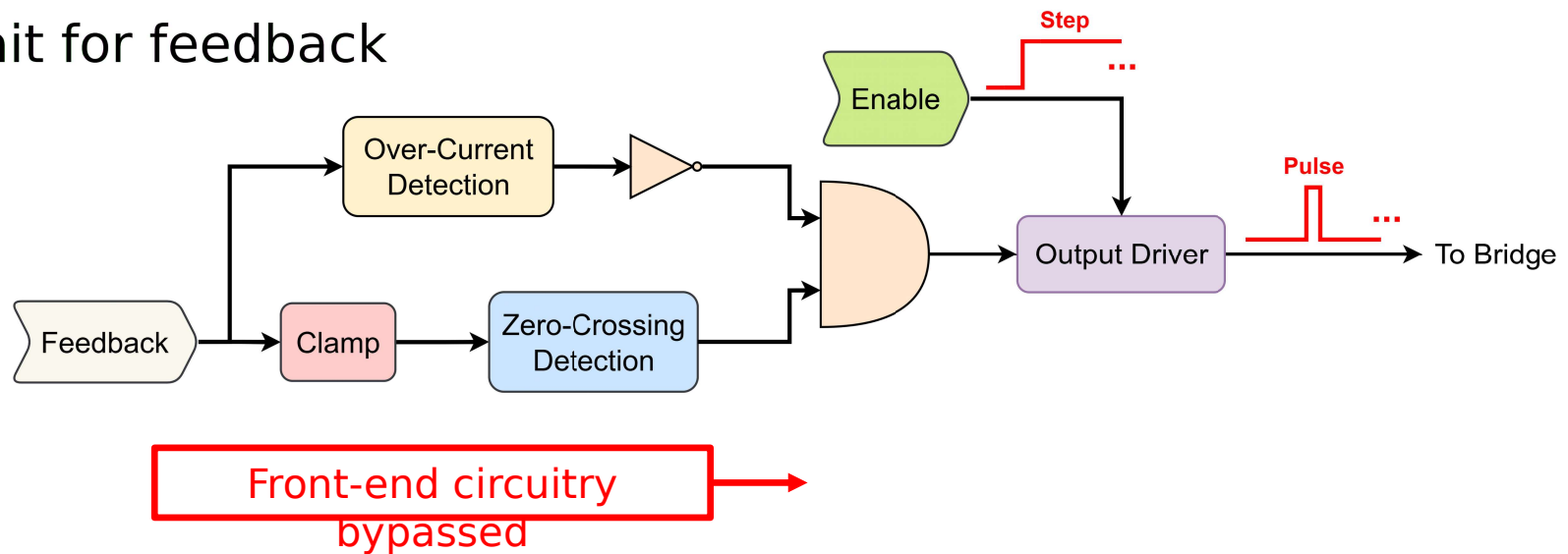
- Upon enable signal, “kickstart” resonant network with pulse
- Wait for feedback



Feedback Driver

Stage 2: Receiving Feedback

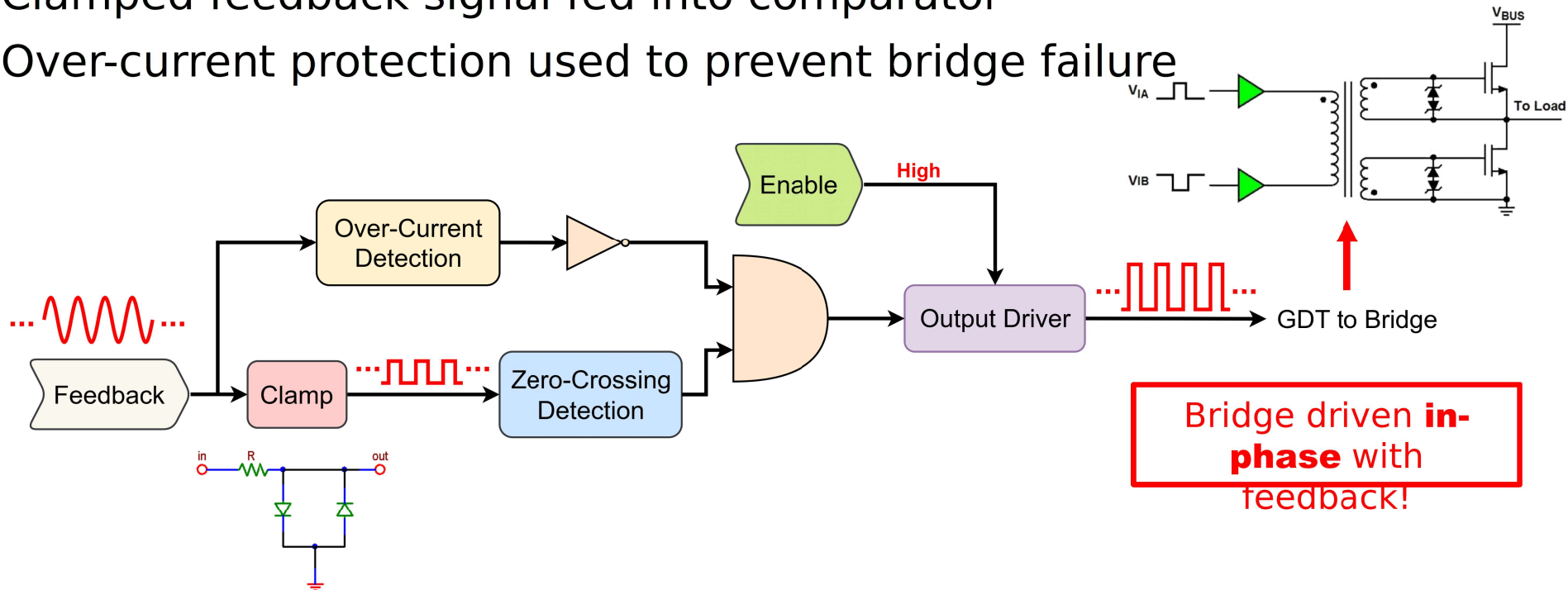
- Clamped feedback signal fed into comparator
- Over-current protection used to prevent bridge failure



Feedback Driver

Stage 3: Turnoff

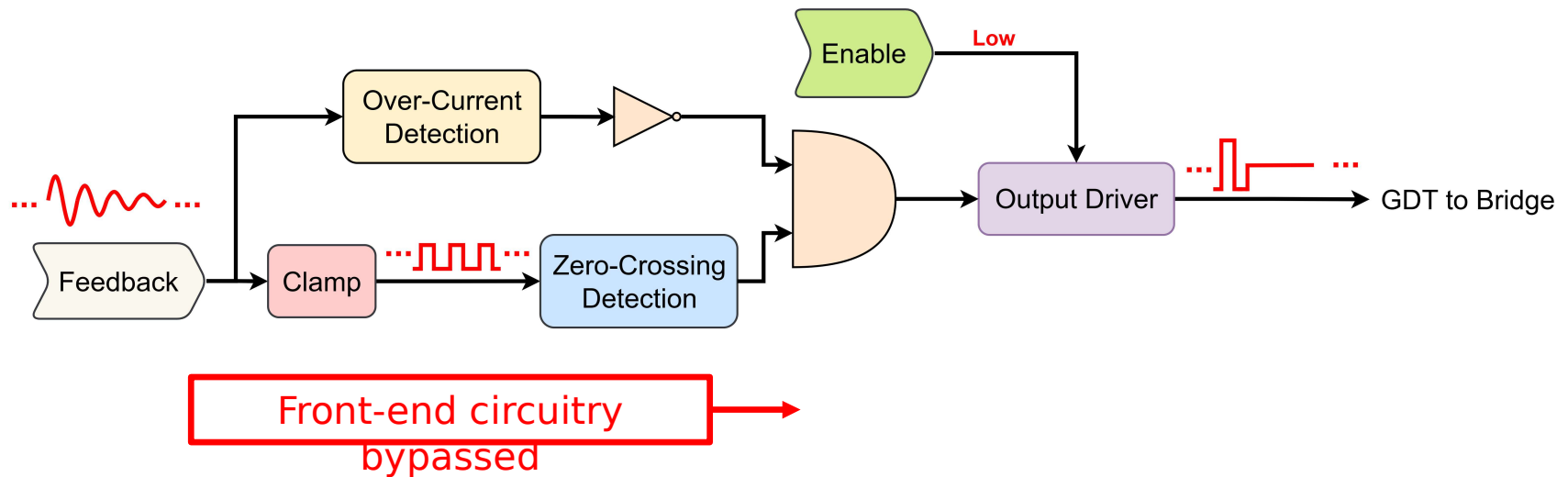- Output disabled at next zero crossing
- LC tank begins ring-down period



Audio Modulation

- Switching enable signal at audible frequency allows coil to play notes!
 - Audio frequencies: 20 Hz – 20 kHz
 - External **“interrupter”** circuit pulses enable signal
- Similar to on-off key (OOK) modulation

1 enable = 1 spark

100 enables/second = 100 sparks/second = 100 Hz tone




Parallel sparks from a modulated DRSSTC,

Loneoceans Laboratories


Interrupter Operation

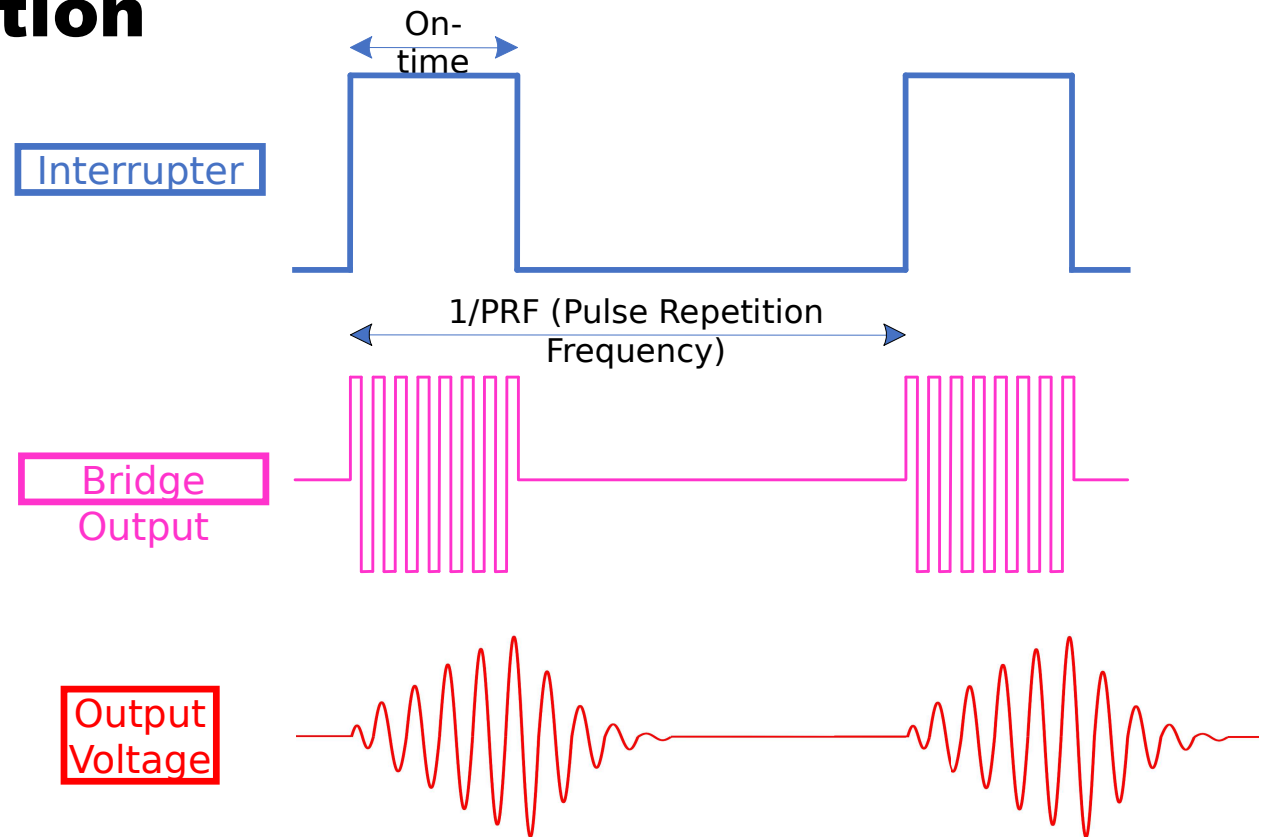- Pulse repetition frequency (PRF) controls tone
- On-time controls duration of spark growth
 - Longer = louder
 - Practically limited to ~5% duty cycle by thermals




Front-End Power Stage/DC Bus

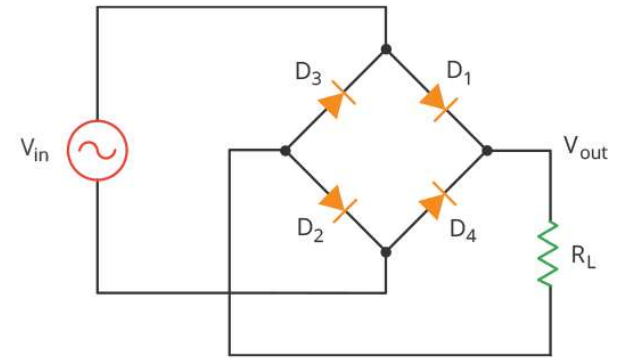- Common to simply rectify mains power
 - Full Bridge (170V) or Doubler (340V)
 - May be influenced by target spark length: $V_{out} = \sqrt{Rb * I_{peak} * V_{in}}$
- Large bus capacitance (~1000s of μF)
- Power factor correction (PFC) can improve efficiency
 - $\sim 0.6 \rightarrow \geq 0.95$ with active PFC




Full Bridge Rectifier

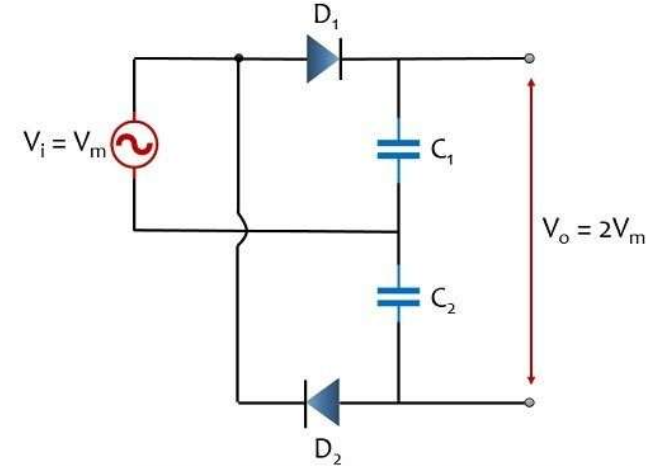

Full Wave Doubler

Power Factor Correction for High Power Inverters, Kaizer Power Electronics

Full System Diagram

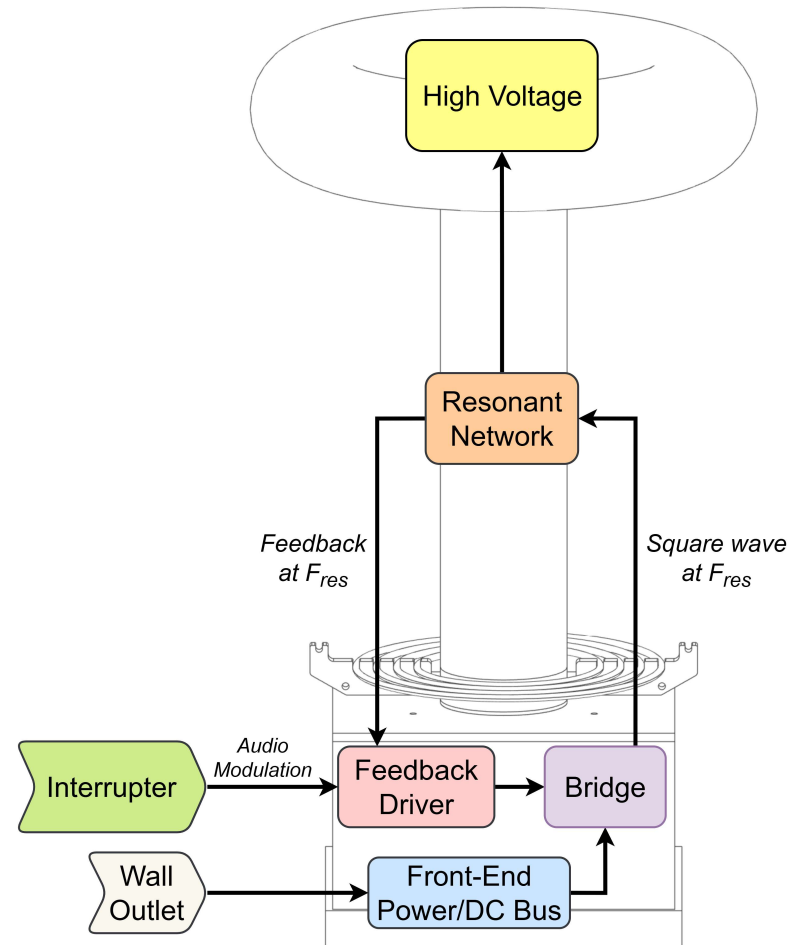

Educational Benefits

Building a Musical DRSSTC requires knowledge of:

- Resonant Circuits and Q Factor
- Impedance Matching
- Frequency Domain and Bode Plots
- Mutual Inductance and Electromagnetism
- Signals and Systems (Fourier Analysis)
- DC→AC and AC→DC Conversion
- Power Semiconductor Devices and Switching Losses
- Thermal Management
- Feedback/Digital Logic/Controls
- Microcontrollers
- Modulation Techniques
- **Making practical design decisions!**

By building a Tesla coil, students can get hands-on experience **before they get to industry!**

Future Plans

Problem:

- Traditional approaches of teaching EM are math-heavy and abstract
 - Students struggle to gain a “practical” understanding of key concepts

Solution:


- One-semester course in which students build Tesla coil
 - Every 1-2 weeks focuses on one concept, lab, and sub-system build
- Target release: Spring 2026, NC State University

Common Reactions:


- “That’s really cool!” *walks away*
- “Have you ever been shocked?”
- “Would it kill you?”
- **“Are there any real-world applications?”**
 - **Well... yes!**

CW/AM Operation

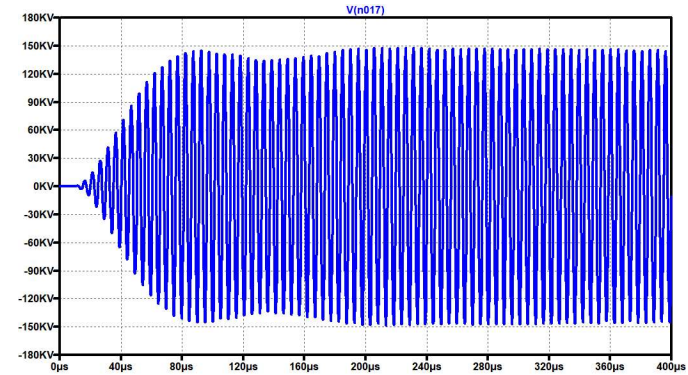- DRSSTC's generally limited to pulse mode by high primary currents
- Reduced currents → continuous wave (CW) operation possible; "steady state"
- PWM of bridge output → AM spark output
 - ~Buck converter at frequency F_{res} , resonant network acts as filter



Resonant startup for CW operation

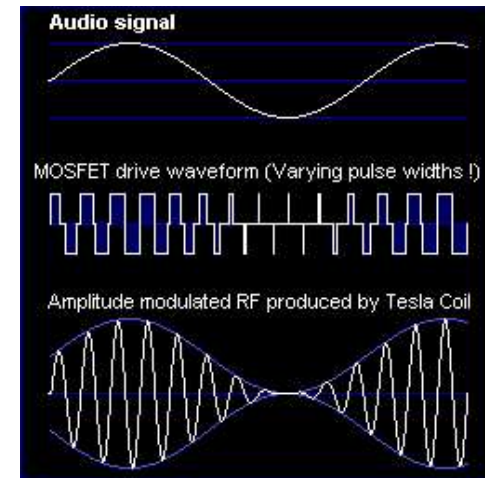


Amplitude modulation of a CW SSTC,

Richie Burnett


Wait. This seems familiar...

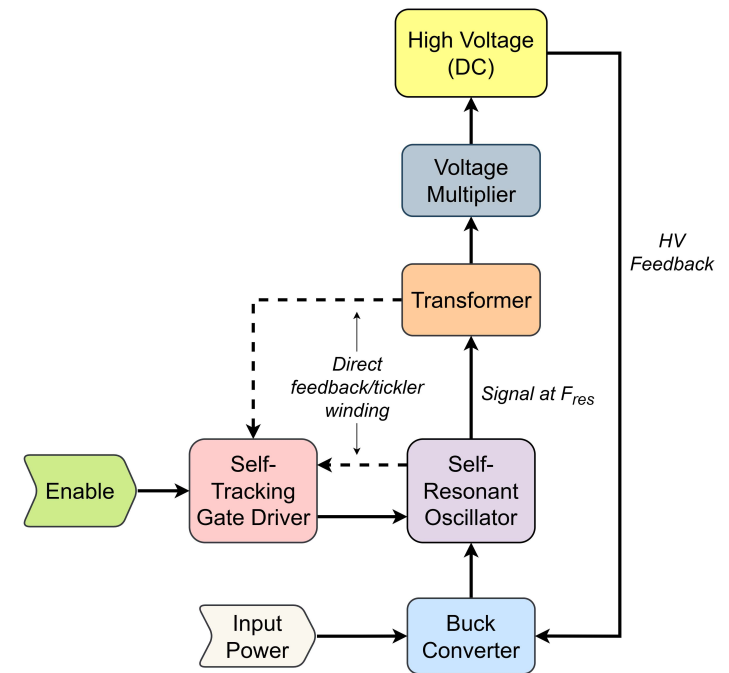- Steady-state, controllable AC output
- Rectify/filter → stable HVDC output
- This is essentially just a resonant power supply!
 - Needs feedback to be self-regulating



“Generalized” Resonant HVPS Architecture

Architecture Comparison

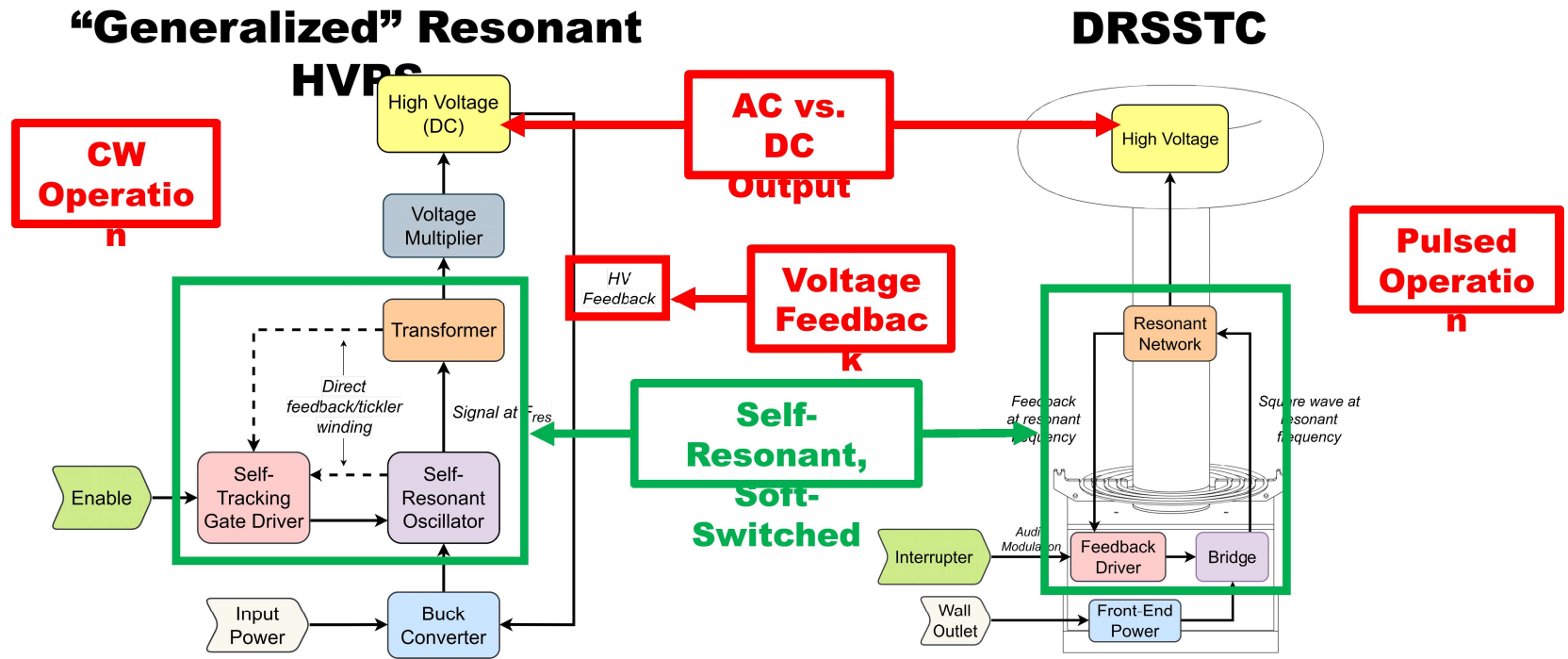

Questions?